
Name:

Western Technical-Commercial School

Date: Section


Series & Parallel Circuit Problems

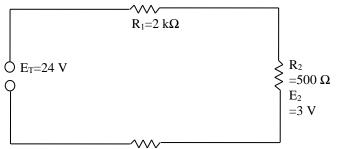Show order of operations, formulas, substitution, units, and all rough work calculations using appropriate units of measure, 2 decimal places, with all answers circled. One mark for the correct answer and one for all work shown. Include double-check to confirm if your answers are correct for full marks.



	Series/Parallel laws							
		L_1	L_2	L_3	L_{T}			
Ohms Law	Εv							
	ΙA							
	RΩ							
	P w							

12

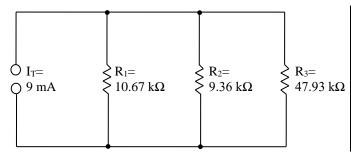

	Series/Parallel laws							
		L_1	L_2	L_3	L_{T}			
Ohms Law	Εv							
	ΙA							
	RΩ							
	Pw							