
Name:

Western Technical-Commercial School


Date: Section
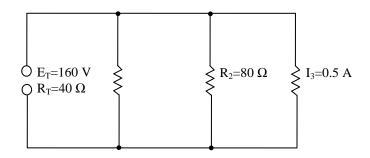
## Parallel Circuit Problems

Show order of operations, formulas, substitution, units, and all rough work calculations using appropriate units of measure, 2 decimal places, with all answers circled. Half mark for the correct answer, the other half for all work shown. **Bonus mark** for properly & correctly double-checking, using a formula not yet used.



	Series/Parallel laws							
		$L_1$	$L_2$	$L_3$	$L_{\mathrm{T}}$			
Ohms Law	Εv							
	ΙA							
	RΩ							
	P w							

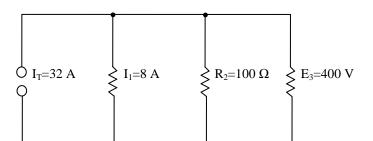

	Series/Parallel laws								
		$L_1$	$L_2$	$L_3$	$L_{T}$				
Ohms Law	Εv								
	ΙA								
	RΩ								
¥	Pw								