

Name:
-------


Western Technical-Commercial School

Date:

Section

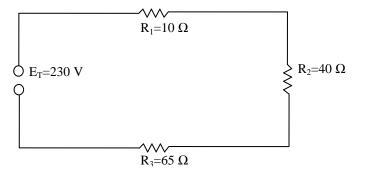
## Series Circuit Problems

Show order of operations, formulas, substitution, units, and all rough work calculations using appropriate units of measure, 2 decimal places, with all answers circled. Half mark for the correct answer, the other half for all work shown. **Bonus mark** for properly & correctly double-checking, using a formula not yet used.



	Series/Parallel laws							
		$L_1$	$L_2$	L <sub>3</sub>	L <sub>T</sub>			
Ohms Law	Εv							
	ΙA							
	RΩ							
	P w							



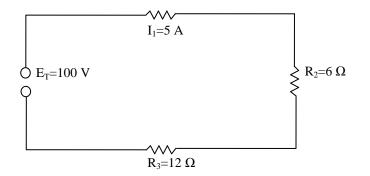

	Series/Parallel laws						
		$L_1$	$L_2$	L <sub>3</sub>	L <sub>T</sub>		
<b>Ohms Law</b>	Εv						
	ΙA						
	RΩ						
	P w						